

Digital electronics and pulse Technique.

Assignment - 02

ID: 21130301221

Question - 01: NAND Gate implementation

using AND & NOT Gate

Logic circuit:

 


Fig: NAND Gate logic circuit.

কোনো একই পাতায় সর্বোচ্চ ১০ টি প্রশ্ন করা যাবে।

voltage table:

| A | B | D ₁ | D ₂ | f ₁ | f ₂ |
|----|----|----------------|----------------|----------------|----------------|
| 0V | 0V | FB | FB | OFF | ON |
| 0V | 5V | FB | RB | OFF | ON |
| 5V | 0V | RB | FB | OFF | ON |
| 5V | 5V | RB | RB | ON | OFF |

fig: voltage table for NAND Gate

Description:

⇒ when A or B both are low (0) then the respective diode or diodes are forward biased. Then the transistor input is low and transistor is off.

So, circuit doesn't conduct.

Hence the output (f₂) is high.

⇒ when A and B both are high the diodes D₁, D₂ are in reverse biased. And we get



high in transistor gate and the transistor become on and current conducts. Hence the output (F_2) is low. now from the voltage table we get a truth table of NAND Gate. Here A & B are our input and F_2 is our output.

Truth table:

| A | B | F |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

fig: Truth table for NAND Gate.

Question - 02: NOR Gate Implementation using OR and NOT Gate.

Logic circuit:

 


fig: Logic circuit for NOR Gate.

voltage table:

| A | B | D ₁ | D ₂ | F ₁ | F ₂ |
|----|----|----------------|----------------|----------------|----------------|
| 0V | 0V | RB | RB | OFF | ON |
| 0V | 5V | RB | FB | ON | OFF |
| 5V | 0V | FB | RB | ON | OFF |
| 5V | 5V | FB | FB | ON | OFF |

fig: voltage table for NOR Gate.

Description:

\Rightarrow when A and B both are low then there no current is flowed by f_2 .

Hence the transistor input is low and it become off and the output f_2 become high.

\Rightarrow when either A or B or both A and B are high then the diode or diodes are forward biased respectively. Then the transistor get high \uparrow input and it become on and current conducts. Hence the output f_2 is low.

Truth table:

| A | B | f_2 |
|---|---|-------|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |

fig: Truth table for NOR Gate.